

Computer Systems

Lecture 22

Overview

- Building computers from logic
- Digital systems
- Digital electronic circuits
- Boolean operations and Boolean gates
- Truth tables for basic logic operations
- Boolean circuits
- Selector circuits

Building computers from logic

- Computer systems may be described at different levels of understanding.
- At the **architectural** level the computer is described as a machine for executing instructions.
 - This level is most appropriate for understanding how programs are executed.
- What about the layers **below** the architectural model?

Engineering level


- Engineering model of the computer represents the machine as a complex electrical circuit.
- Within the circuit there are a large number of physical connections, along each of which a current may flow during the operation of the machine.
 - Presence of a current is used to represent transmission of the binary digit **1**, while
 - Absence of a current represents a value **0**.

Digital Systems

- Digital systems based on electronic circuitry
 - 1s and 0s, or on and off
 - Each 1 or 0 is called a bit; or binary digit
 - Computers use digital data representation

Digital Signal


- 1001011...

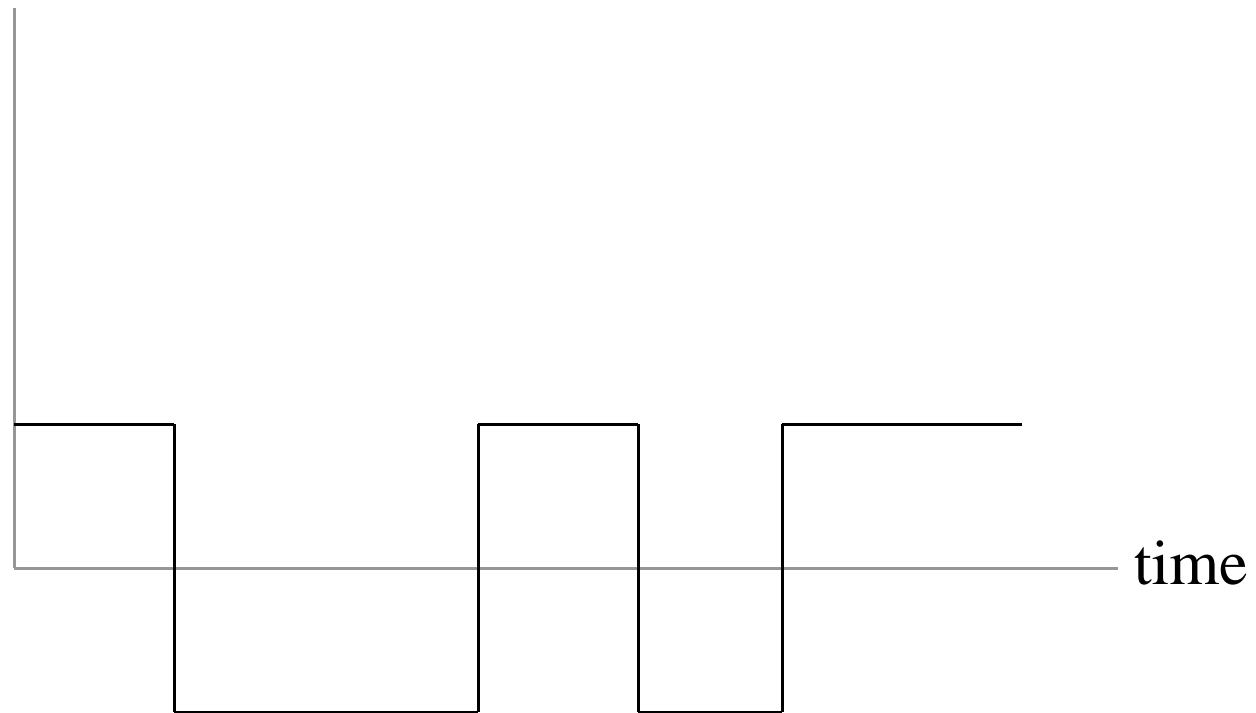

Digital electronic circuit

- This kind of circuit is called **digital electronic** circuit, because the relevant characteristic is the presence or absence of current (digit 1 or 0), rather than the amount of current flowing.

Analog Signal

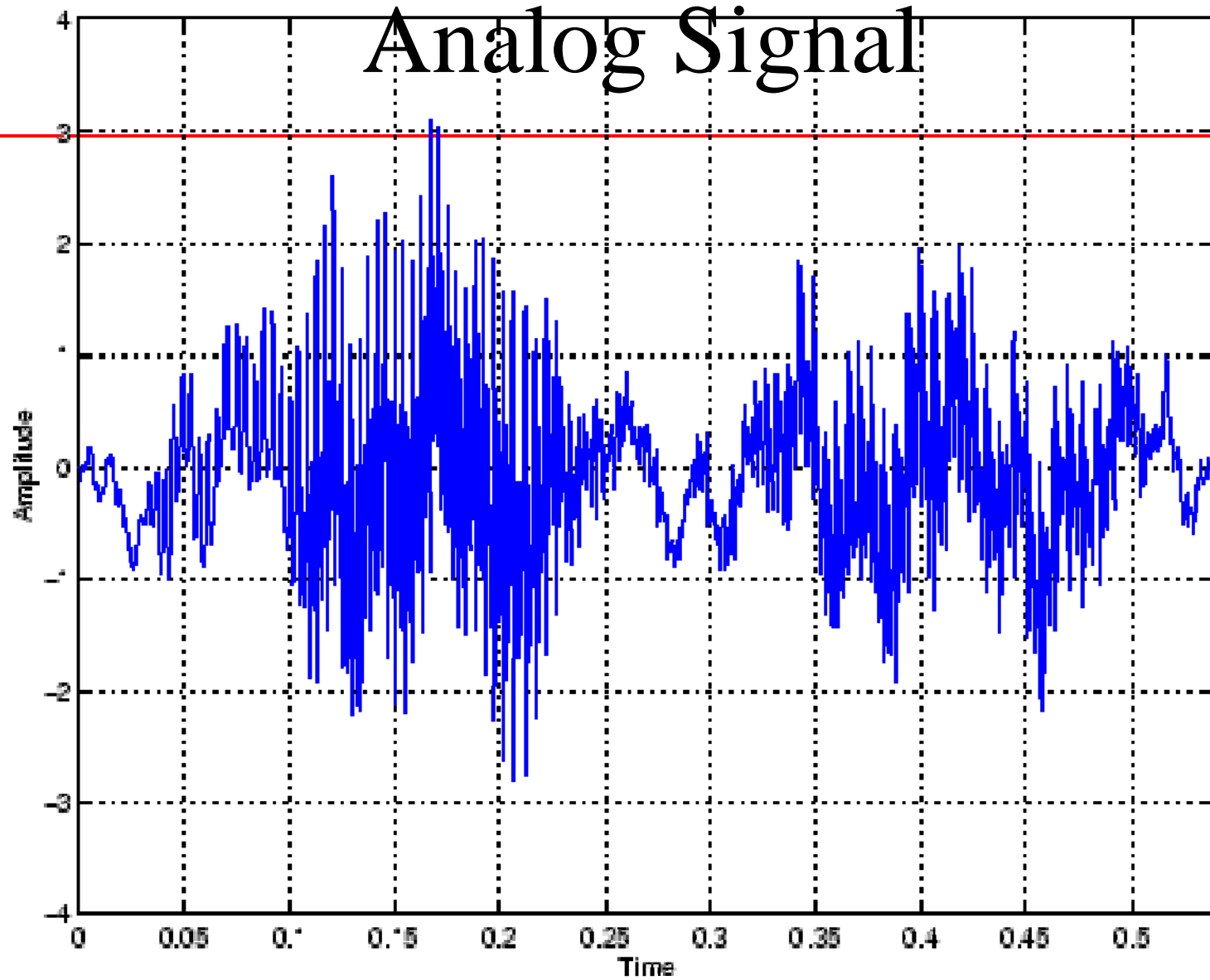

Analog Systems

- Analog
 - continuously variable values, along a range, such as
 - temperature and
 - pressure values
 - traditional analog recording devices are
 - humidity recorders,
 - mercury thermometers, and
 - pressure gauges
 - standard telephone lines transmit analog signals

Boolean Operations and Boolean Gates

- All operations that computers perform may be defined in terms of **basic boolean functions, operating on bits**.
- The digital electronic circuits and their components can be built from the devices implementing basic boolean operations – **boolean gates** (logic gates).

Boolean Gates

- Consider the circuit device called **AND gate**:



- Two of these, labelled *A* and *B*, represents electronic **inputs** to the component, along each of which a current may
 - flow (boolean value 1) or may
 - not flow (boolean value 0).
- Third connection, labelled *Y* represents the **output** of the component.

AND gate

- In the case of AND gate current will flow in Y if and only if a current flows in the input A **and** in the input B .



- One may write $Y = A$ **and** B .
- Thus, this component implements logic (boolean) operation **AND**.

Truth tables for basic logic operations

A B	A and B	A B	A or B	A	not A
0 0	0	0 0	0	0	1
0 1	0	0 1	1	1	0
1 0	0	1 0	1		
1 1	1	1 1	1		

A B	A xor B	A B	A = B
0 0	0	0 0	1
0 1	1	0 1	0
1 0	1	1 0	0
1 1	0	1 1	1

Alternative notations

- **and:** \wedge , **&**
- **or:** \vee
- **xor:** $|$
- **not:** \neg , **-**

Boolean gates

- Other standard logic gate drawing representations:



OR gate




NOT gate




XOR gate

Basic logic gates and their truth tables


Inputs		C
A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1

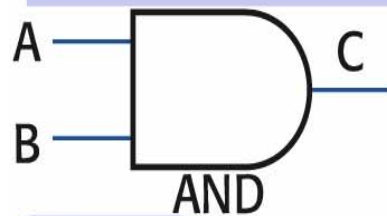

Inputs		A OR B
A	B	A OR B
0	0	0
0	1	1
1	0	1
1	1	1

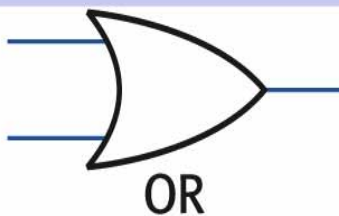

Inputs		A XOR B
A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0

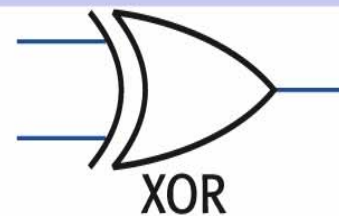

Inputs	NOT A
A	NOT A
0	1
1	0

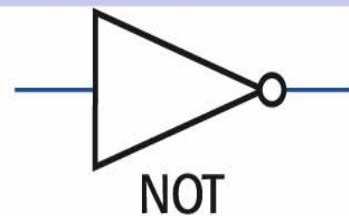


Fig. 4.2 Basic digital logic gates.

© Pearson Education 2001

More boolean gates




NAND gate, $Y = \mathbf{not} (A \mathbf{and} B)$




NOR gate, $Y = \mathbf{not} (A \mathbf{or} B)$

Three-input gates


2-input AND gate

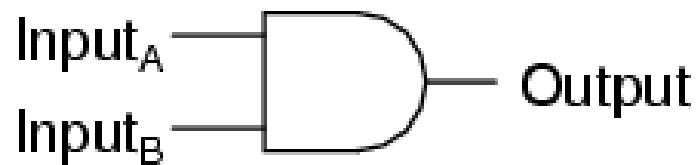


3-input AND gate

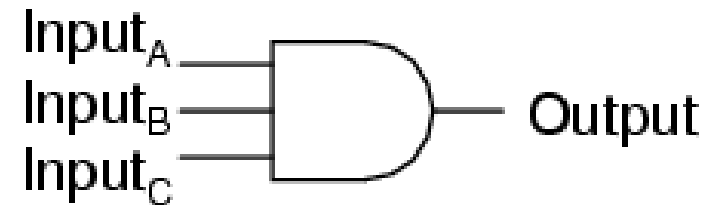

2-input OR gate

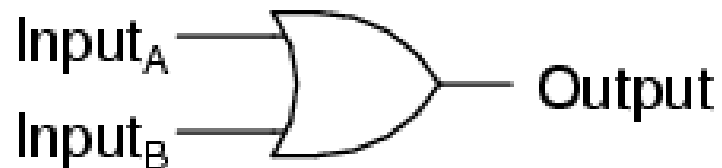

3-input OR gate

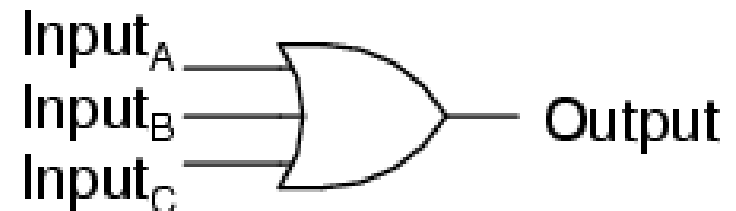

Boolean circuits

- Elementary boolean gates can be combined into **boolean circuits**, implementing more complex **boolean functions** (operations).
- In fact, any boolean function can be implemented with this set of basic boolean gates.

Examples of circuits

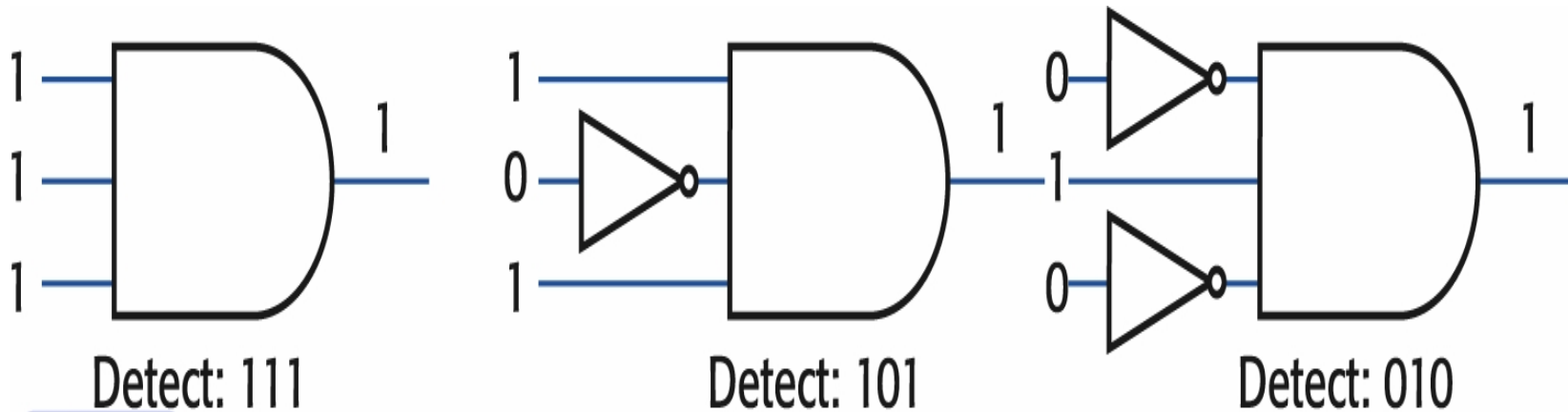


Fig. 4.3 Using AND gates to detect specific bit patterns.

© Pearson Education 2001

Exercise

- Draw Boolean circuits to implement detectors that detect the presence of the following inputs
 - 000
 - 110

Data flow control circuit - Filter

D X	Out
0 0	0
0 1	0
1 0	0
1 1	1


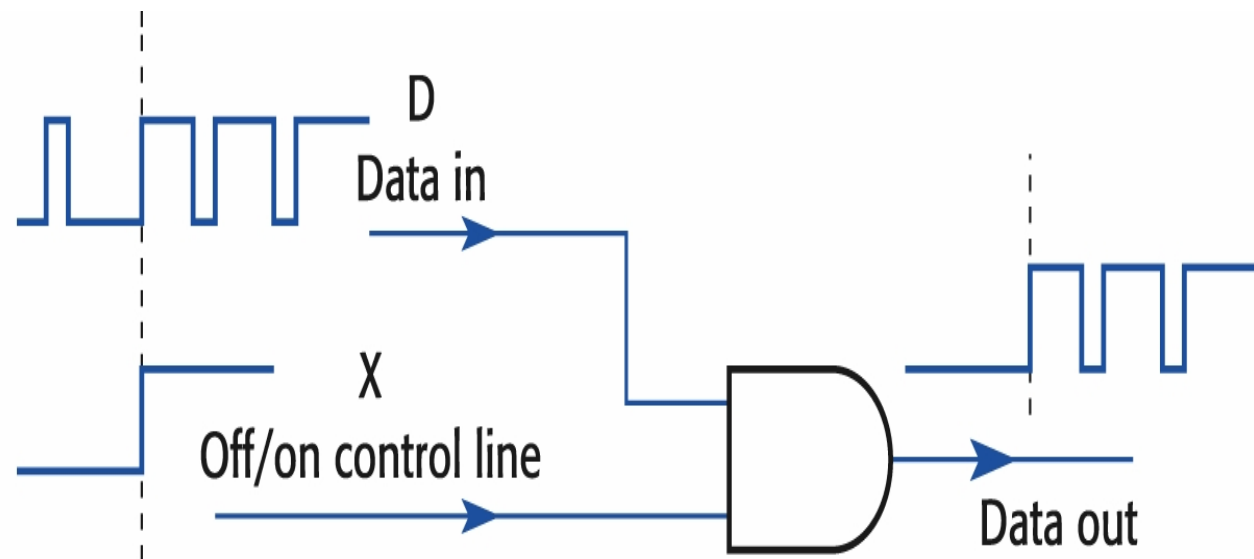


Fig. 4.4 Data flow control circuit.

© Pearson Education 2001

Selector circuit

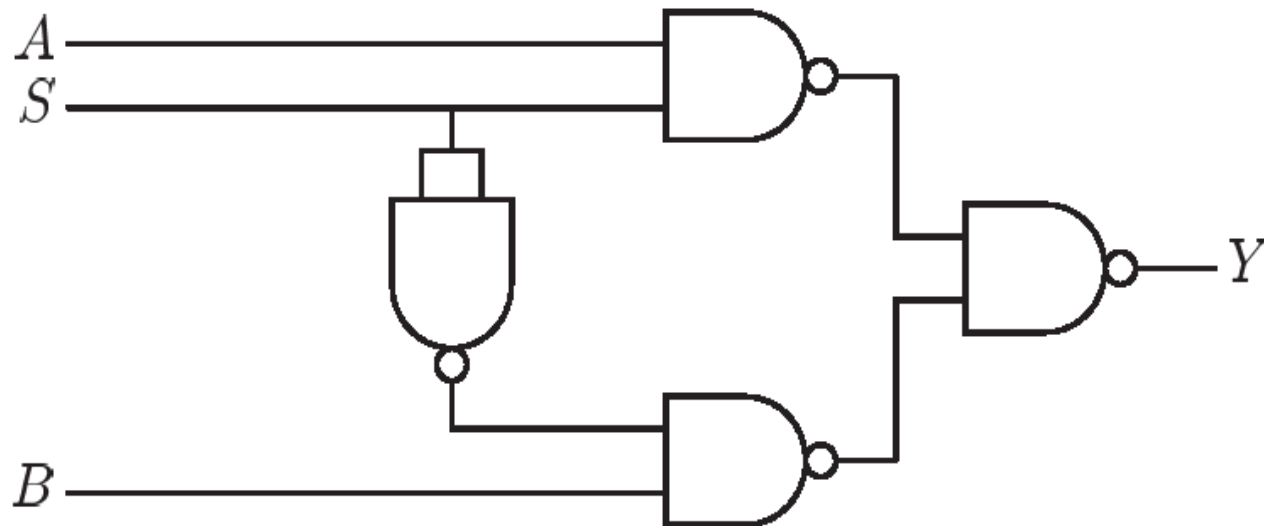

If $S = 1$ then $Y = A$

if $S = 0$ then $Y = B$

Ex. Build the truth table for the selector circuit and verify its functions.

Readings

- [Wil06] Chapter 4, sections 4.1 - 4.2.